

JEE Main Exercise

1. (D)

$$R = R_0(1 + \alpha\Delta T)$$

$$60 = 20[1 + \alpha(500 - 20)]$$

$$\alpha = \frac{1}{240}/^{\circ}\text{C}$$

$$R = R_0(1 + \alpha\Delta T)$$

$$\Rightarrow 25 = 20\left(1 + \frac{1}{240}(T - 20)\right)$$

$$\Rightarrow T = 80^{\circ}\text{C}$$

2. (C)

At  $0^{\circ}\text{C}$ ,  $R_1 = 400\Omega$ ,  $R_2 = 800\Omega$

$$R_{eq} = \frac{400 \times 800}{400 + 800} = \frac{800}{3}\Omega$$

At  $t^{\circ}\text{C}$ ,

$$\frac{1}{R'_{eq}} = \frac{1}{R'_1} + \frac{1}{R_2}$$

$$\frac{1}{\frac{800}{3}(1 + \alpha_{eq}t)} = \frac{1}{400(1 + \alpha t)} + \frac{1}{400(1 + 4\alpha t)}$$

$$\Rightarrow \frac{3}{800}(1 - \alpha_{eq}t) = \frac{1}{400}(1 - \alpha t) + \frac{1}{800}(1 - 4\alpha t)$$


$$\Rightarrow \frac{3\alpha_{eq}t}{800} = \frac{\alpha t}{400} + \frac{4\alpha t}{800}$$

$$\Rightarrow \alpha_{eq} = 2\alpha$$

3. (C)

$$i = \frac{Q}{T} = \frac{Q}{\left(\frac{2\pi}{\omega}\right)} = \frac{Q\omega}{2\pi}$$

4. (D)




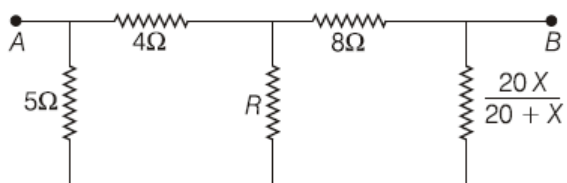


For equivalent resistance to be independent of  $R$ , it should be a balanced Wheatstone bridge.

$$\Rightarrow 4 \left( \frac{20X}{20+X} \right) = 8 \times 5$$


$$\Rightarrow x = 20 \Omega$$

5. (A)

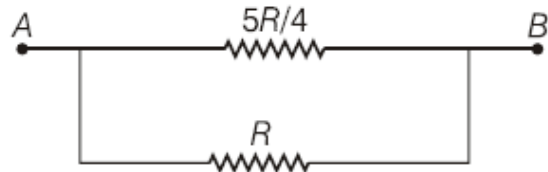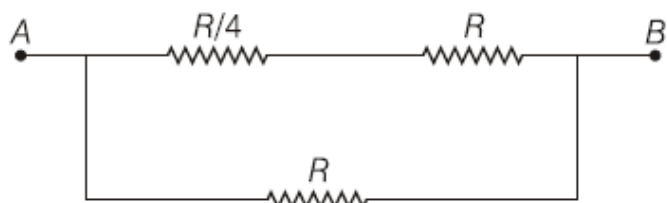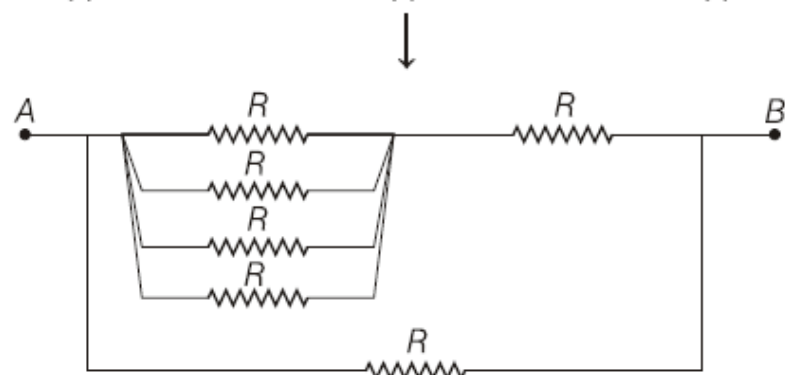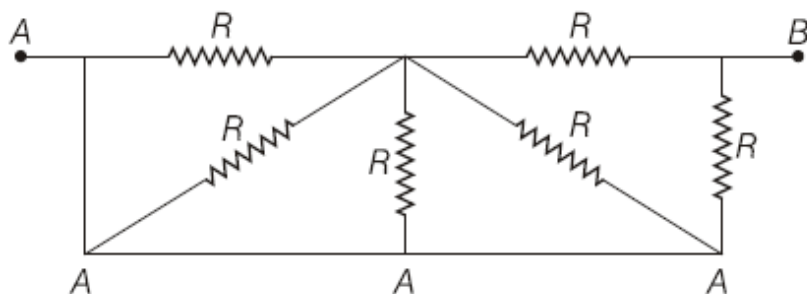

$$\frac{1}{R_{eq}} = \frac{1}{5R} + \frac{1}{R}$$

$$\Rightarrow R_{eq} = \frac{5R}{9}$$

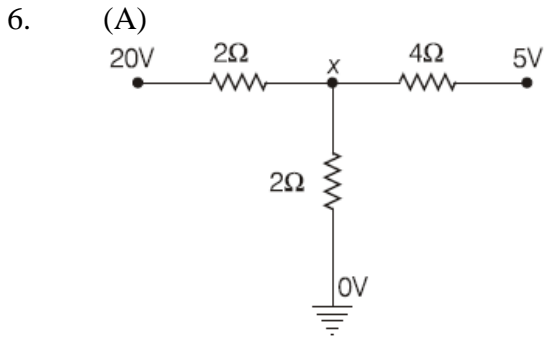

Lets take potential of junction to be  $x$ .

Applying KCL at the junction,


$$\frac{20-x}{2} + \frac{5-x}{4} + \frac{0-x}{2} = 0$$

$$\Rightarrow 40 - 2x + 5 - x - 2x = 0$$

$$x = 9 \text{ V}$$

$$\text{Current through the switch} = \frac{x-0}{2}$$

$$= \frac{9-0}{2} = 4.5 \text{ A}$$

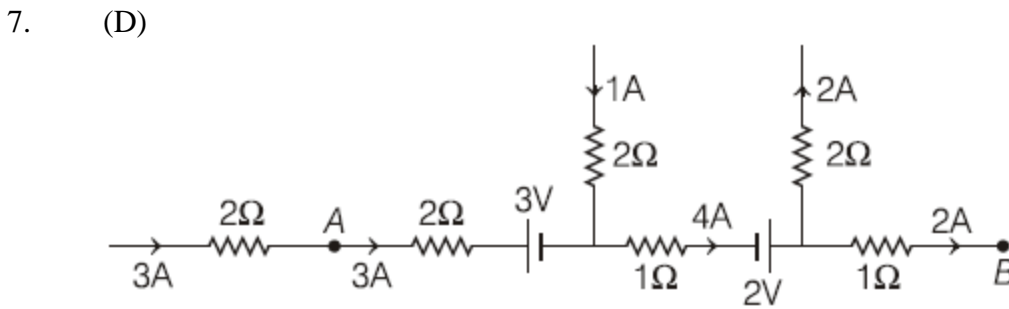

$$V_A - 3(2) - 3 - 4(1) + 2 - 2(1) = V_B$$

$$\Rightarrow V_A - V_B = 13 \text{ V}$$

8. (A)  
Lets take potential of the junction to be  $x$ .


Using KCL at the junction,

$$\frac{10-x}{1} + \frac{10-x}{1} + \frac{10-x}{1} = 9$$


$$\Rightarrow x = 7 \text{ V}$$

$$\frac{x - V_D}{\frac{4}{3}} = 9 \Rightarrow 7 - V_D = 12$$

$$\Rightarrow V_D = -5 \text{ V}$$

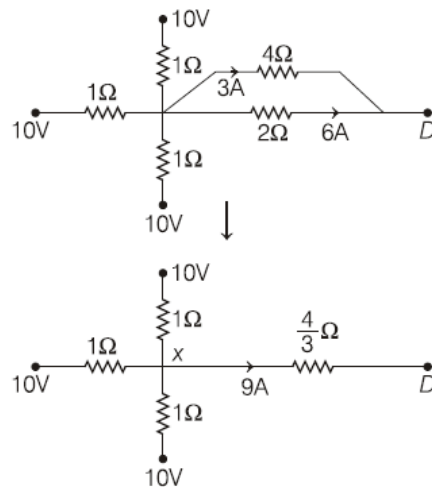


9. (B)

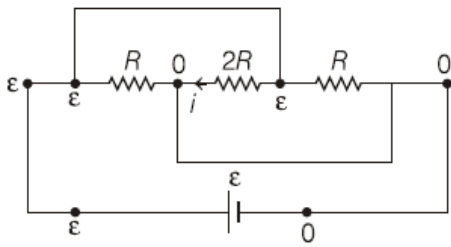


Current in a resistor flows from high potential to low potential. So, current in  $2R$  resistance will be from right to left.

10. (B)

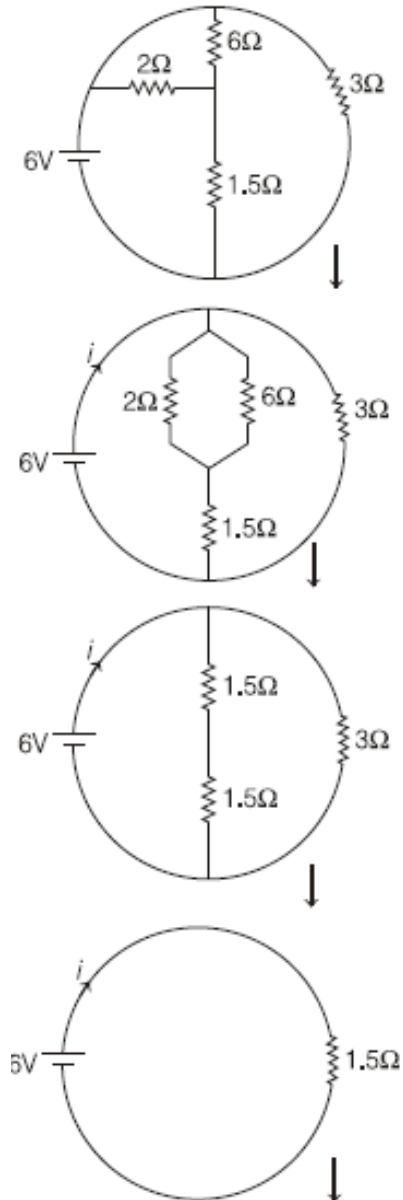

$$i = \frac{6}{1.5} = 4 \text{ A}$$

11. (B)

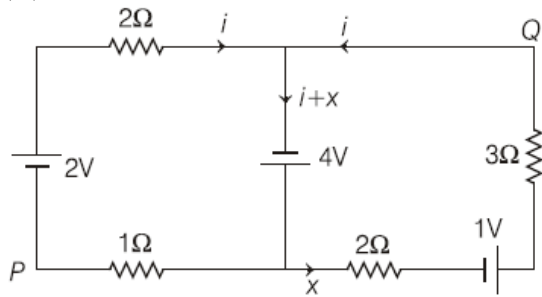

Using KVL,

$$+2 - 2i + 4 - i(1) = 0$$

$$\Rightarrow i = 2 \text{ A}$$


$$+4 - 2x + 1 - 3x = 0$$

$$\Rightarrow x = 1 \text{ A}$$

$$V_P + 2 - i(2) = V_Q$$

$$\Rightarrow V_P - V_Q = 2i - 2 = 2(2) - 2 = 2 \text{ V}$$

12. (B)

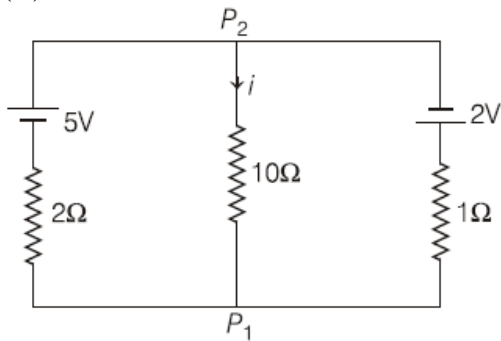


$$\epsilon_{eq} = \frac{\frac{\epsilon_1 + \epsilon_2}{\frac{1}{r_1} + \frac{1}{r_2}}}{\frac{1}{2} + \frac{1}{1}} = \frac{\frac{5 - 2}{\frac{1}{2} + \frac{1}{1}}}{\frac{1}{2} + \frac{1}{1}} = \frac{1}{3} \text{ V}$$

$$r_{eq} = \frac{r_1 r_2}{r_1 + r_2} = \frac{2}{3} \Omega$$

$$i = \frac{\epsilon_{eq}}{R + r_{eq}} = \frac{\frac{1}{3}}{10 + \frac{2}{3}} = \frac{1}{32} \text{ A} = 0.03 \text{ A}$$

13. (D)

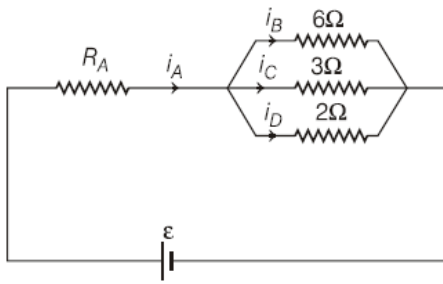


$$i_B : i_C : i_D = \frac{1}{R_B} : \frac{1}{R_C} : \frac{1}{R_D}$$

$$= \frac{1}{6} : \frac{1}{3} : \frac{1}{2} = 1 : 2 : 3$$

$$i_A = i_B + i_C + i_D$$

$$\Rightarrow i_A : i_B : i_C : i_D = 6 : 1 : 2 : 3$$


14. (B)

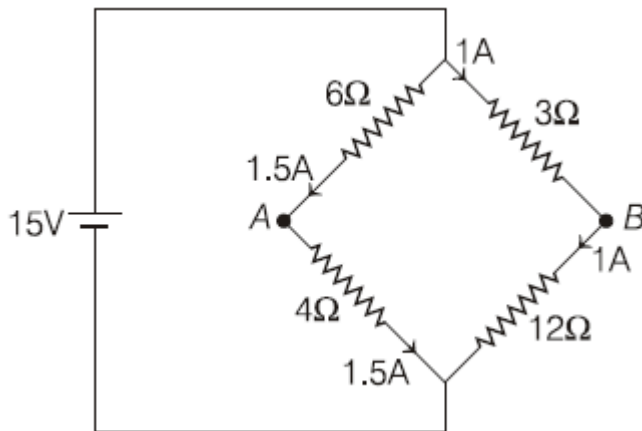

$$V_A - 1.5(4) + 1(12) = V_B$$

$$V_A - V_B = -6 \text{ V}$$


15. (C)

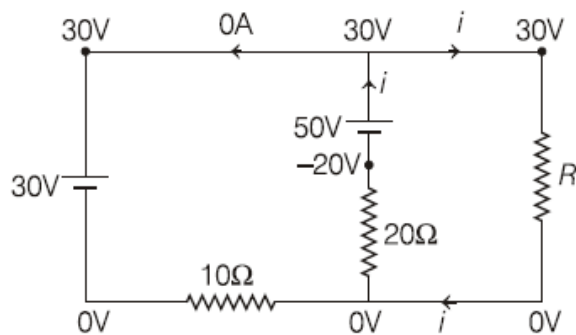

$$i = \frac{0 - (-20)}{20} = \frac{30 - 0}{R}$$

$$\Rightarrow R = 30\Omega$$

16. (D)

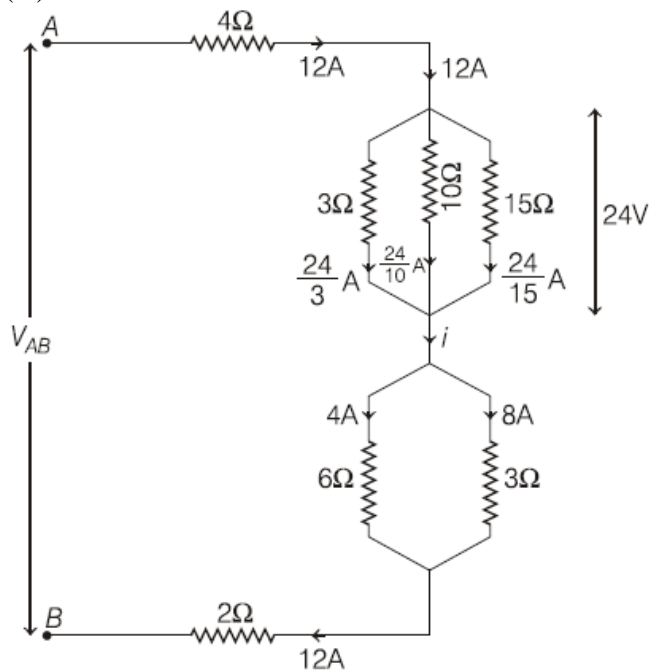


$$i = \frac{24}{15} + \frac{24}{10} + \frac{24}{3} = 12 \text{ A}$$

$$V_{AB} = 12(4) + 24 + 8(3) + 12(2) = 120 \text{ V}$$

$$\text{Current through } 6\Omega \text{ resistor} = \frac{3}{3+6}(12) = 4 \text{ A}$$

17. (C)

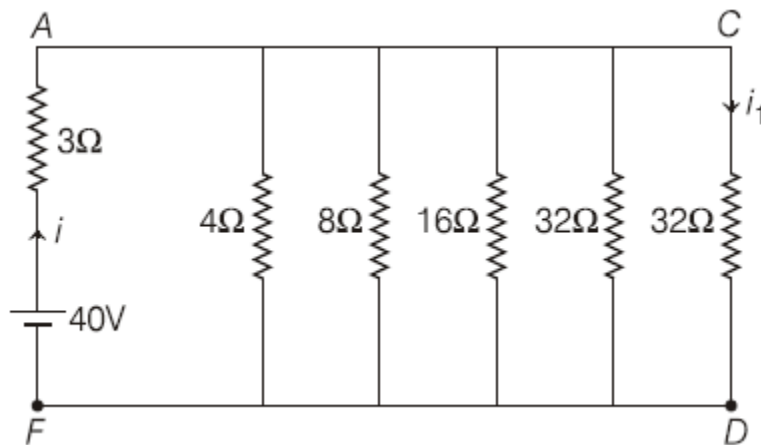

$$R_{\text{eq}} = 3 + \left( \frac{1}{4} + \frac{1}{8} + \frac{1}{16} + \frac{1}{32} + \frac{1}{32} \right)^{-1} = 3 + 2 = 5 \Omega$$


$$i = \text{Current through battery} = \frac{40}{5} = 8 \text{ A}$$

$$i_1 = \left( \frac{\frac{1}{32}}{\frac{1}{4} + \frac{1}{8} + \frac{1}{16} + \frac{1}{32} + \frac{1}{32}} \right) (8)$$

$$i_1 = \frac{1}{2}$$

$$\frac{i_1}{i} = \frac{1/2}{8} = \frac{1}{16}$$

18. (A)

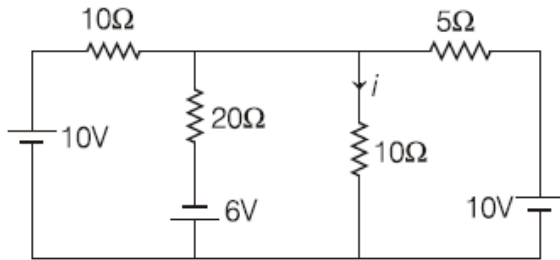

$$\varepsilon_{\text{eq}} = \frac{\frac{\varepsilon_1}{r_1} + \frac{\varepsilon_2}{r_2} + \frac{\varepsilon_3}{r_3}}{\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3}}$$

$$= \frac{\frac{10}{10} - \frac{6}{20} + \frac{10}{5}}{\frac{1}{10} + \frac{1}{20} + \frac{1}{5}} = \frac{54}{7} \text{ V}$$

$$i = \frac{\varepsilon_{\text{eq}}}{R + r_{\text{eq}}} = \frac{\frac{54}{7}}{10 + \frac{20}{7}}$$


$$= \frac{54}{90} = \frac{3}{5} = 0.6 \text{ A}$$

19. (D)

Resistance of an ideal voltmeter is infinite.

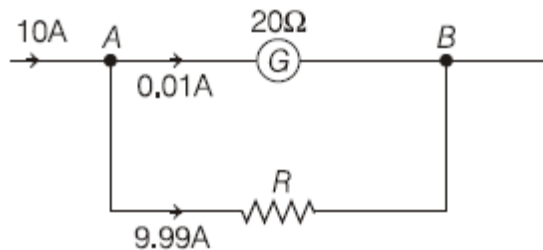20. (B)

Full scale deflection current  $= i_g = \frac{0.2}{20} = 0.01 \text{ A}$






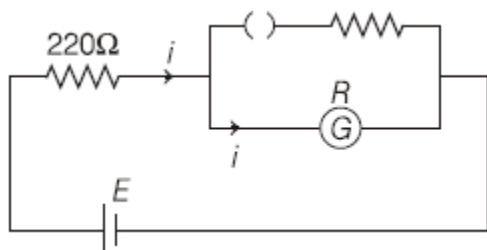21. (D)

For galvanometer,  $i \propto \theta$


If deflection becomes  $\left(\frac{1}{5}\right)$ th, then current through galvanometer will also become  $\left(\frac{1}{5}\right)$ th.



When  $K_1$  is closed and  $K_2$  is open, let current through the galvanometer be  $i$ .

Let  $R$  be resistance of the galvanometer.

$$\Rightarrow i = \frac{E}{220 + R}$$

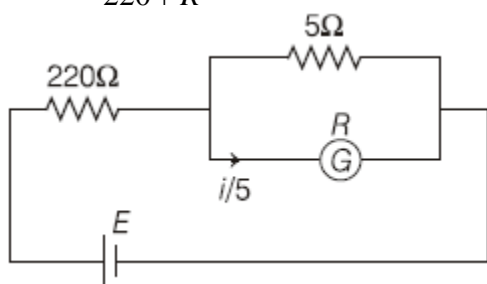

When  $K_2$  is also closed, current through the galvanometer becomes  $\frac{i}{5}$ .

$$\frac{i}{5} = \left( \frac{E}{220 + \frac{5R}{5+R}} \right) \left( \frac{5}{5+R} \right)$$

$$\Rightarrow \frac{1}{5} \left( \frac{E}{220 + R} \right) = \left( \frac{E}{220 + \frac{5R}{5+R}} \right) \left( \frac{5}{5+R} \right)$$

$$\Rightarrow R = 22 \Omega$$

22. (D)

$$V = i_g (R_G + R)$$


$$\Rightarrow 20 = i_g (R_G + 1680) \quad \dots(i)$$

$$\Rightarrow 30 = i_g (R_G + 2930) \quad \dots(ii)$$

Solving Eqs. (i) and (ii), we get

$$R_G = 820 \Omega \text{ and } i_g = 8 \text{ mA}$$

23. (B)

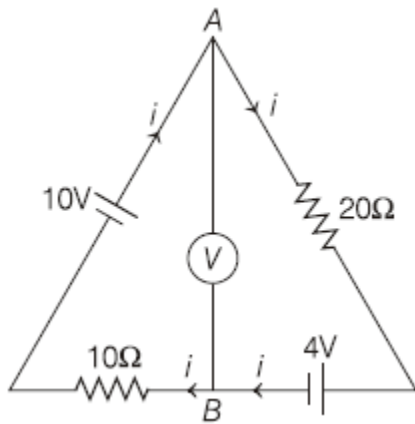

Ideal voltmeter has infinite resistance, so current through voltmeter is nearly zero.

Applying KVL in the loop,


$$+10 - 20i - 4 - 10i = 0$$

$$\Rightarrow i = 0.2 \text{ A}$$

$$V_A - 20(0.2) - 4 = V_B$$

$$V_A - V_B = 8 \text{ V}$$

24. (A)

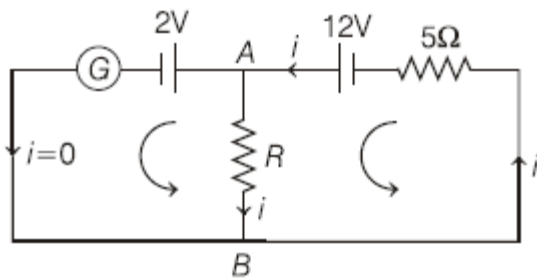

Applying KVL,


$$+12 - iR - 5i = 0$$

$$i = \frac{12}{R+5}$$

$$V_A - 2 = V_B \Rightarrow V_A - V_B = 2$$

$$\Rightarrow \left( \frac{12}{R+5} \right) R = 2 \Rightarrow R = 1 \Omega$$

25. (A)

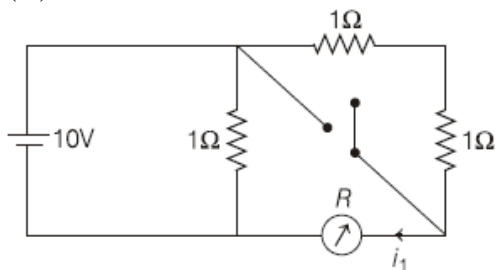


Let the resistance of the ammeter be  $R$ .

When the switch is open,

$$\text{Reading of ammeter} = i_1 = \frac{10}{R+2}$$

When the switch is closed.

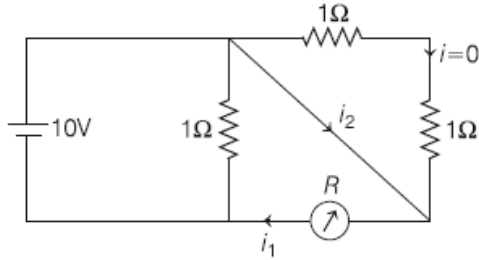


$$i_2 = \frac{10}{R}$$

$$i_2 = 2i_1$$

$$\Rightarrow \frac{10}{R} = 2 \left( \frac{10}{R+2} \right)$$

$$\Rightarrow R = 2\Omega$$

26. (C)

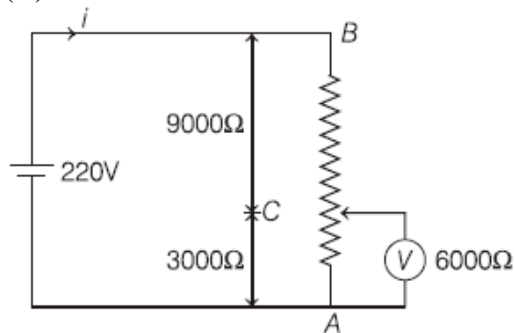

$$R_{CA} = \frac{1}{4}(12000) = 3000\Omega$$

$$R_{BC} = \frac{3}{4}(12000) = 9000\Omega$$

$$i = \frac{220}{900 + \frac{6000 \times 3000}{6000 + 3000}} = 0.02\text{ A}$$

$$\text{Reading voltmeter} = (0.02) \left( \frac{6000 \times 3000}{6000 + 3000} \right) = 40\text{ V}$$

27. (A)

From the graph,

When  $G \rightarrow \infty$ ,  $V = 20\text{ V}$

Potential difference across resistor when  $G \rightarrow \infty$

$$= \left( \frac{24}{R+1} \right) R = 20$$

$$\Rightarrow 6R = 5R + 5$$

$$\Rightarrow R = 5\Omega$$

28. (B)

For balanced Wheatstone bridge,

$$6(625) = QS$$

$$\Rightarrow \frac{P}{Q} = \frac{S}{625} \quad \dots(i)$$

After interchanging  $P$  and  $Q$ , condition for the balanced Wheatstone bridge,

$$Q(625+51) = PS$$

$$\Rightarrow \frac{P}{Q} = \frac{676}{S} \quad \dots(ii)$$

From Eqs. (i) and (ii), we get

$$\frac{S}{625} = \frac{676}{S}$$

$$\Rightarrow S = \sqrt{625 \times 676} = 25 \times 26 = 650 \Omega$$

29. (5)

$$R = \frac{\rho l}{A}$$

$$R' = \frac{\rho(1+\alpha_1\Delta T)/(1+\alpha_2\Delta T)}{A(1+2\alpha_1\Delta T)}$$


$$R' = \frac{\rho l}{A} (1+\alpha_1\Delta T)(1-\alpha_2\Delta T)$$



$$R' = R(1+(\alpha_1-\alpha_2)\Delta T)$$

Temperature coefficient of resistance =  $\alpha_1 - \alpha_2$

$$= 6 \times 10^{-3} - 1 \times 10^{-3} = 5 \times 10^{-3}$$

30. (5)


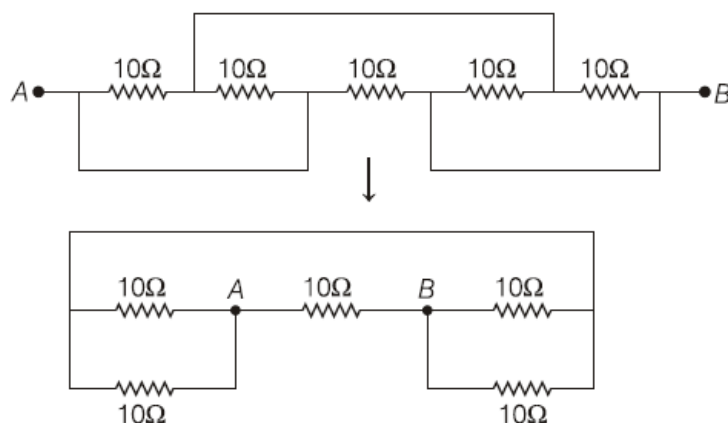


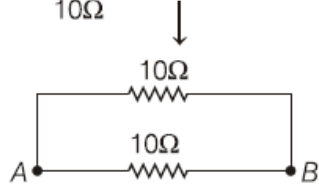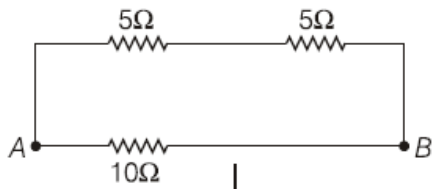


$$\frac{1}{R_{eq}} = \frac{1}{10} + \frac{1}{10} \Rightarrow R_{eq} = 5 \Omega$$

31.

(4)

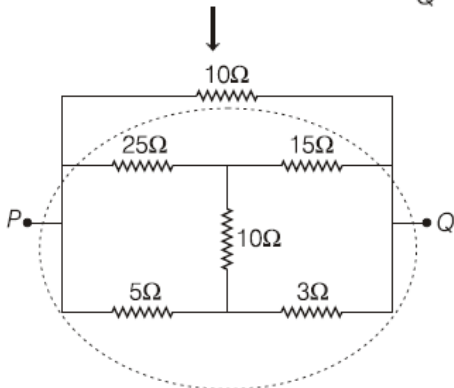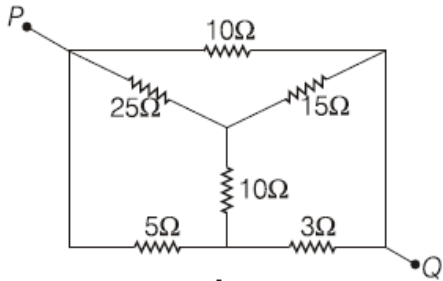


Balanced Wheatstone bridge

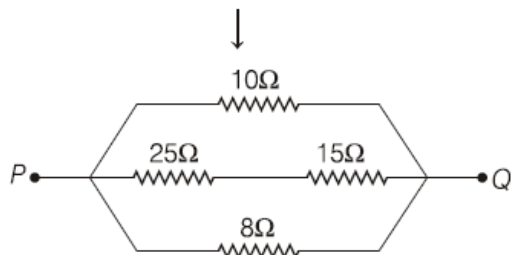

$$\frac{1}{R_{eq}} = \frac{1}{10} + \frac{1}{40} + \frac{1}{8}$$

$$\Rightarrow R_{eq} = 4 \Omega$$

32. (9)

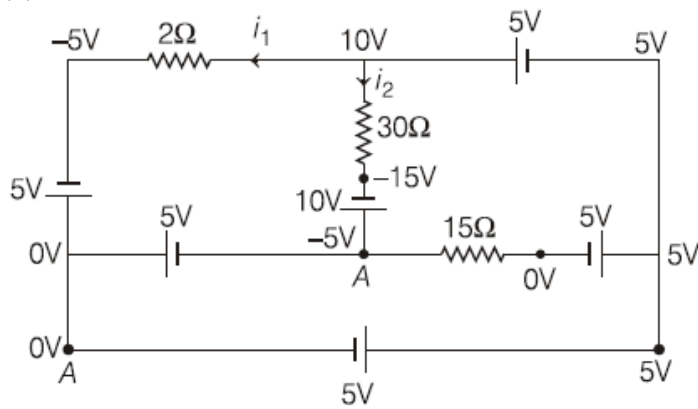


Lets take  $V_A = 0 \text{ V}$

$$i_1 = \frac{10 - (-5)}{2} = 7.5 \text{ A}$$

$$i_2 = \frac{10 - (-15)}{30} = \frac{5}{6} \text{ A}$$

$$\frac{i_1}{i_2} = \frac{\frac{15}{2}}{\frac{5}{6}} = 9$$

33. (5)

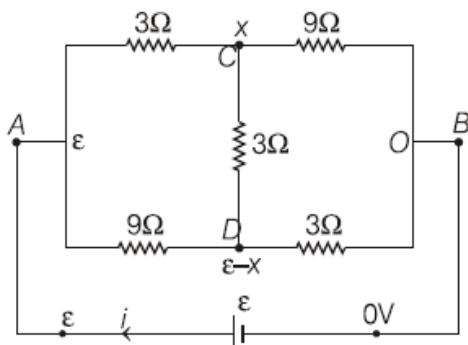

Due to cross-symmetry, current through both  $3 \Omega$  resistances will be same. So, potential difference across both  $3 \Omega$  resistances will be also same.

Applying KCL at junction C,

$$\frac{\varepsilon - x}{3} + \frac{0 - x}{9} + \frac{(\varepsilon - x) - x}{3} = 0$$


$$\Rightarrow 3\varepsilon - 3x - x + 3\varepsilon - 6x = 0$$

$$\Rightarrow x = \frac{3\varepsilon}{5}$$


$$i = \frac{\varepsilon - x}{3} + \frac{\varepsilon - (\varepsilon - x)}{9} = \frac{2\varepsilon}{15} + \frac{\varepsilon}{15} = \frac{\varepsilon}{5}$$

$$R_{\text{eq}} = \frac{\varepsilon}{i} = 5 \Omega$$

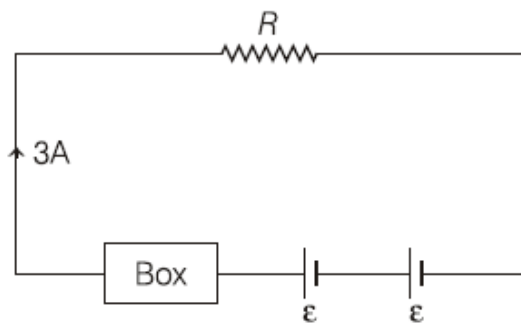34. (1)  
 Lets take number of cells wrongly connected in the box to be  $n$ .  
 Equivalent emf of the box  $= (12 - n)\epsilon - n\epsilon = (12 - 2n)\epsilon$



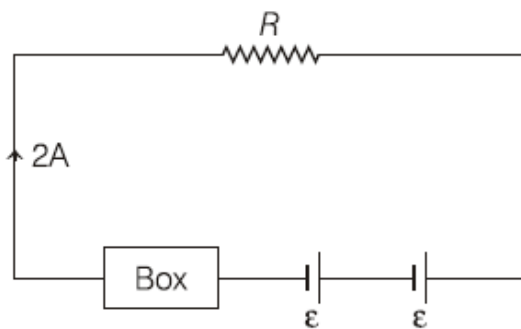
$$3 = \frac{(12 - 2n)\epsilon + 2\epsilon}{R} \quad \dots(i)$$



$$2 = \frac{(12 - 2n)\epsilon - 2\epsilon}{R} \quad \dots(ii)$$

Solving Eqs. (i) and (ii), we get  
 $n = 1$

35. (6)

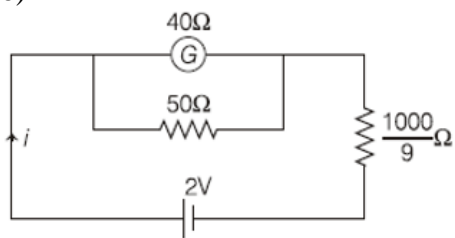


$$\begin{aligned} \text{Current through galvanometer} &= \left( \frac{50}{50 + 40} \right) \times (15 \text{ mA}) \\ &= \frac{25}{3} \text{ mA} \end{aligned}$$

$$\text{Current sensitivity} = \frac{50}{\frac{25}{3}} = 6 \text{ div/mA}$$

$$\begin{aligned} i &= \frac{2}{\frac{1000}{9} + \left( \frac{40 \times 50}{40 + 50} \right)} \\ &= 158 \times 10^{-3} \text{ A} \\ &= 15 \text{ mA} \end{aligned}$$

36. (2)

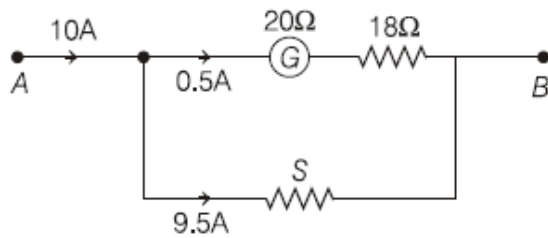


For half scale deflection, current through the galvanometer = 0.5 A

$$V_A - V_B = 0.5(20 + 18) = 9.5(S)$$

$$\Rightarrow S = 2\Omega$$

37. (30)

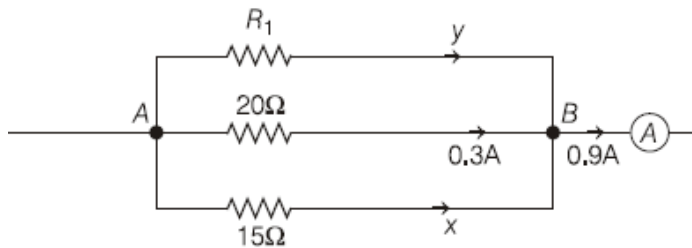


$$V_A - V_B = 20(0.3) = x(15) \Rightarrow x = 0.4 \text{ A}$$

$$x + y + 0.3 = 0.9 \Rightarrow y = 0.2 \text{ A}$$

$$V_A - V_B = 20 = (0.2)R_1$$

$$\Rightarrow R_1 = 30\Omega$$

38. (7)

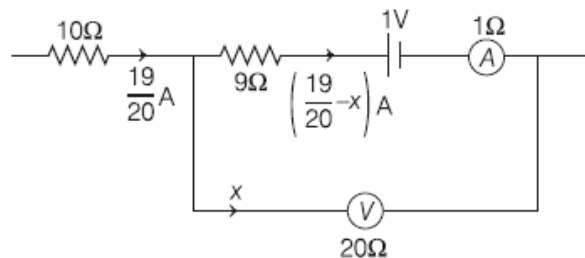


Using KVL in the loop,

$$-9\left(\frac{19}{20} - x\right) - 1 - 1\left(\frac{19}{20} - x\right) + 20x = 0$$

$$\Rightarrow x = 0.35 \text{ A}$$

$$\text{Reading of voltmeter} = x(20) = 0.35 \times 20 = 7 \text{ V}$$

39. (6600)

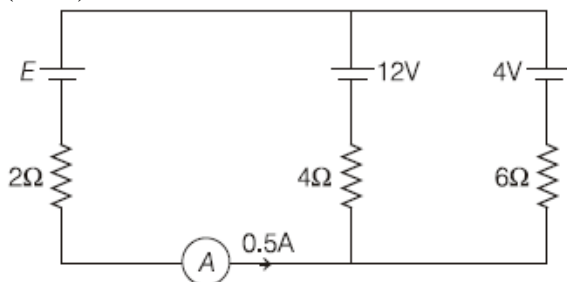




$$\epsilon_{\text{eq}} = \frac{\frac{12}{4} + \frac{4}{6}}{\frac{1}{4} + \frac{1}{6}} = \frac{44}{5} \text{ V}$$

$$\frac{1}{r_{\text{eq}}} = \frac{1}{4} + \frac{1}{6}$$
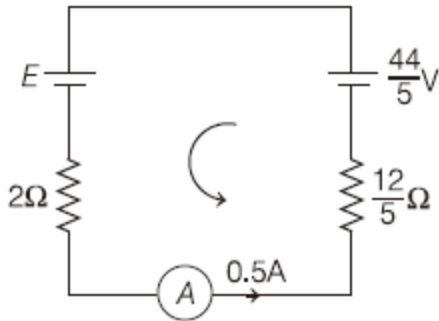
$$\Rightarrow r_{\text{eq}} = \frac{12}{5} \Omega$$




Applying KVL in the loop,

$$+\frac{44}{5} - E - 2(0.5) - \frac{12}{5}(0.5) = 0$$

$$\Rightarrow E = 6.6 \text{ V} = 6600 \text{ mV}$$

40. (80)

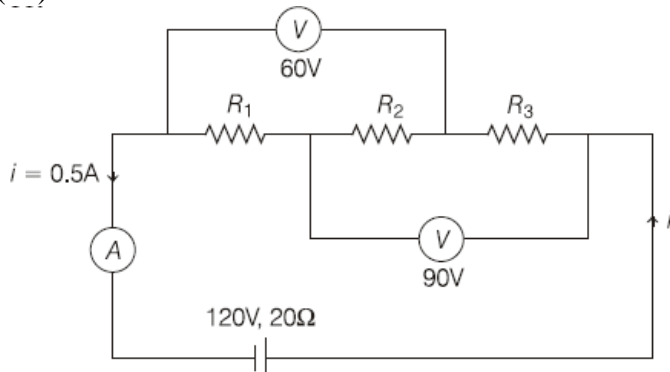

$$i(R_1 + R_2) = 60$$

$$\Rightarrow 0.5(R_1 + R_2) = 60$$

$$\Rightarrow R_1 + R_2 = 120 \Omega \quad \dots(\text{i})$$

$$i(R_2 + R_3) = 90$$

$$\Rightarrow 0.5(R_2 + R_3) = 90$$

$$\Rightarrow R_2 + R_3 = 180 \Omega \quad \dots(\text{ii})$$

$$i = \frac{120}{R_1 + R_2 + R_3 + 20} = 0.5$$

$$\Rightarrow R_1 + R_2 + R_3 = 220 \quad \dots(\text{iii})$$

Solving Eqs. (i), (ii) and (iii), we get

$$R_2 = 80 \Omega$$

41. (3)  
Let balance length be  $l$  and unknown resistance be  $R$ .

For null point,

$$2(100 - l) = R(l) \quad \dots(i)$$

When  $2\Omega$  and  $R$  are interchanged, balance point shifts by 20 cm.

So, for null point,


$$R(100 - (l + 20)) = 2(l + 20)$$

$$\Rightarrow R(80 - l) = 2(l + 20) \quad \dots(ii)$$

Solving Eqs. (i) and (ii), we get

$$l = 40 \text{ cm and } R = 3\Omega$$

42. (3)

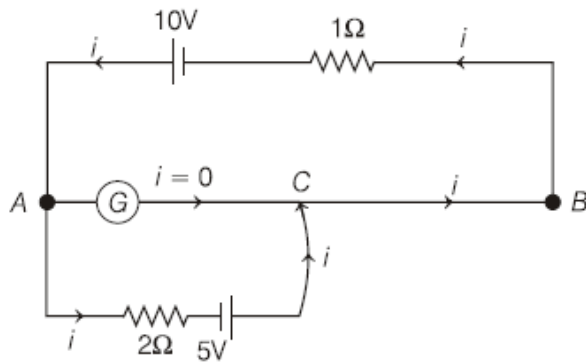

Applying KVL,

$$-i + 10 - 2i + 5 - iR_{BC} = 0$$

$$\Rightarrow i = \frac{15}{3 + R_{BC}}$$

$$V_A - V_C = 5 - 2i = 0$$

$$\Rightarrow i = 2.5 \text{ A}$$

$$2.5 = \frac{15}{3 + R_{BC}}$$

$$\Rightarrow R_{BC} = 3\Omega$$

43. (0.2)

$$\text{Current in the primary circuit} = \frac{3}{10 + 20} = 0.1 \text{ A}$$

$$\begin{aligned} \text{Potential drop across the potentiometer wire} \\ = 0.1 \times 20 = 2 \text{ V} \end{aligned}$$

$$x = \text{potential gradient} = \frac{2}{10} = 0.2 \text{ V/m} = 0.2 \text{ mV/mm}$$

For balance point,

$$V = xl$$

$$\Delta V = x\Delta l = \left(0.2 \frac{\text{mV}}{\text{mm}}\right)(1 \text{ mm}) = 0.2 \text{ mV}$$

1. (A)  
In electric circuit ammeter is connected in series with resistance and voltmeter parallel with the net resistance.  
In ohm's law, we check  $V = IR$  by varying net resistance of the circuit.

2. (B)  
(b) Resistance between P and Q

$$r_{PQ} = r \parallel \left( \frac{r}{3} + \frac{r}{2} \right) = \frac{r \times \frac{5}{6}r}{r + \frac{5}{6}r} = \frac{5}{11}r$$

Resistance between Q and R

$$r_{QR} = \frac{r}{2} \parallel \left( r + \frac{r}{3} \right) = \frac{\frac{r}{2} \times \frac{4}{3}r}{\frac{r}{2} + \frac{4}{3}r} = \frac{4}{11}r$$

Resistance between P and R

$$r_{PR} = \frac{r}{3} \parallel \left( \frac{r}{2} + r \right) = \frac{\frac{r}{3} \times \frac{3}{2}r}{\frac{r}{3} + \frac{3}{2}r} = \frac{3}{11}r$$

Hence, it is clear that  $r_{PQ}$  is maximum.


3. (C)  
(c) As 200 V battery is charging

$$\text{So, } 220 = 200 + i \cdot 1$$

$$i = 20 \text{ A}$$


$$\text{So, } 20 \times R = 220 \text{ V}$$

$$\Rightarrow R = 11 \Omega$$

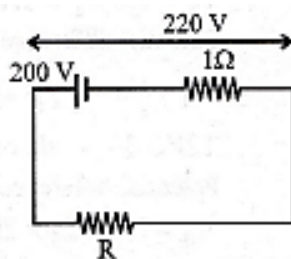

4. (C)  
(c)  $\frac{100}{R+r} = \frac{90}{R} \Rightarrow \frac{R+r}{R} = \frac{10}{9} \Rightarrow 1 + \frac{0.5}{R} = \frac{10}{9}$   
 $\Rightarrow \frac{0.5}{R} = \frac{1}{9} \therefore R = 4.5 \Omega$

5. (D)

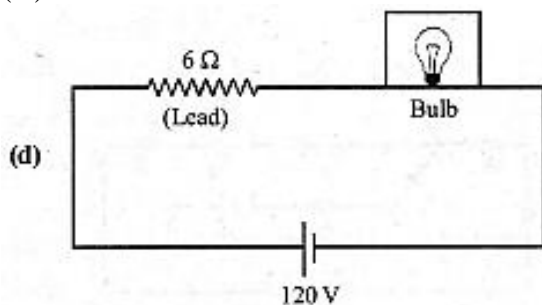

Power of bulb = 60 W (given)

$$\text{Resistance of bulb} = \frac{120 \times 120}{60} = 240 \Omega \quad \left[ \because P = \frac{V^2}{R} \right]$$

Power of heater = 240 W (given)

$$\text{Resistance of heater} = \frac{120 \times 120}{240} = 60 \Omega$$

Voltage across bulb before heater is switched on,

$$V_1 = \frac{240}{246} \times 120 = 117.73 \text{ volt}$$

Voltage across bulb after heater is switched on,

$$V_2 = \frac{48}{54} \times 120 = 106.66 \text{ volt}$$

Hence decrease in voltage

$$V_1 - V_2 = 117.073 - 106.66 = 10.04 \text{ Volt (approximately)}$$

6. (C)

(c) Total power consumed by electrical appliances in the building,  $P_{\text{total}} = 2500 \text{ W}$

Watt = Volt  $\times$  ampere

$$\Rightarrow 2500 = V \times I \Rightarrow 2500 = 220 I$$

$$\Rightarrow I = \frac{2500}{220} = 11.36 \approx 12 \text{ A}$$

(Minimum capacity of main fuse)

7. (C)

(c) Current in each bulb =  $\frac{\text{Power}}{\text{Voltage}} = \frac{100}{220} = 0.45 \text{ A}$

Current through ammeter =  $0.45 \times 3 = 1.35 \text{ A}$

8. (B)

$$(b) \quad V = IR = (neAv_d)\rho \frac{\ell}{A} \quad \therefore \rho = \frac{VA}{n_e AV_d \ell} = \frac{V}{n_e V_d \ell}$$

Here  $V$  = potential difference

$\ell$  = length of wire

$n$  = no. of electrons per unit volume of conductor.

$e$  = no. of electrons

Placing the value of above parameters we get resistivity

$$\rho = \frac{5}{8 \times 10^{28} \times 1.6 \times 10^{-19} \times 2.5 \times 10^{-4} \times 0.1} = 1.6 \times 10^{-5} \Omega m$$

9. (C)


$$(c) \quad i = neAV_d \text{ and } V_d \propto \sqrt{E} \text{ (Given)}$$

$$\text{or, } i \propto \sqrt{E} \text{ or, } i^2 \propto E \text{ or, } i^2 \propto V$$

Hence graph (c) correctly depicts the  $V$ - $I$  graph for a wire made of such type of material.

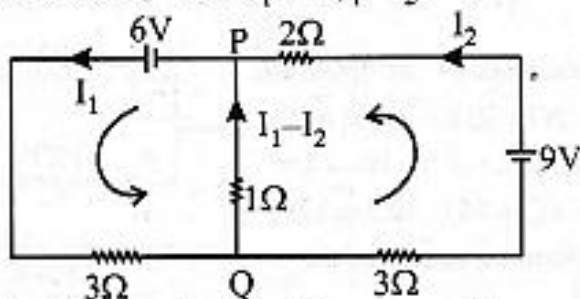10. (A)

$$(a) \quad \text{From KVL, } -6 + 3I_1 + 1(I_1 - I_2) = 0$$



$$6 = 3I_1 + I_1 - I_2; \quad 4I_1 - I_2 = 6 \quad \dots(i)$$

$$-9 + 2I_2 - (I_1 - I_2) + 3I_2 = 0$$

$$-I_1 + 6I_2 = 9 \quad \dots(ii)$$

On solving (i) and (ii)

$$I_1 = 0.13A$$

Direction Q to P, since  $I_1 > I_2$ .

11. (C)

$$(c) \quad i = \frac{V}{R + \frac{Rr}{R+r}} \times \left( \frac{R}{R+r} \right) = \frac{V}{R+2r}$$

$$\text{So, } P = i^2 R = \frac{V^2 R}{(R+2r)^2}$$

for  $H_{\max}$ ,  $P$  is maximum

$$\frac{dp}{dr} = 0 \Rightarrow \frac{(R+2r)^2 - 2(R+2r) \cdot 2r}{(R+2r)^4} = 0$$

$$\Rightarrow (R+2r)(R+2r-4r) = 0$$

$$\Rightarrow r = -\frac{R}{2} \text{ or } r = \frac{R}{2} \Rightarrow r = \frac{R}{2} \text{ so, } f = \frac{1}{2}$$

12. (A)

Given  $R_1 = 100\Omega$ ,  $r' = r/2$ ,  $R_2 = ?$

Resistivity of wire,  $R = \frac{\rho l}{A} \because \text{Area} \times \text{lenght} = \text{volume}$

$$\text{Hence, } R = \frac{\rho V}{A^2}$$

Since,  $\rho \rightarrow \text{constant}$ ,  $V \rightarrow \text{constant}$

$$R \propto \frac{1}{A^2} \text{ OR } R \propto \frac{1}{r^4} \because A = \pi r^2$$

$$\frac{R_2}{R_1} = 16 \Rightarrow R_2 = 16 \times 100 = 1600\Omega, \text{ Resistance of new wire.}$$

13. (A)

(a) In steady state, flow of current through capacitor will be zero.


Current through the circuit,

$$i = \frac{E}{r+r_2}$$

Potential difference through capacitor

$$V_c = \frac{Q}{C} = E - ir = E - \left( \frac{E}{r+r_2} \right) r$$

$$\therefore Q = CE \frac{r_2}{r+r_2}$$

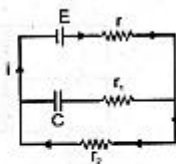

14. (B)

The potential difference in each loop is zero.

$\therefore$  No current will flow or current in each resistance is zero


15. (D)

(d) There is no change in null point, if the cell and the galvanometer are exchanged in a balanced wheatstone bridge.

On balancing condition  $\frac{R_1}{R_3} = \frac{R_2}{R_4}$


After exchange  
On balancing condition

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

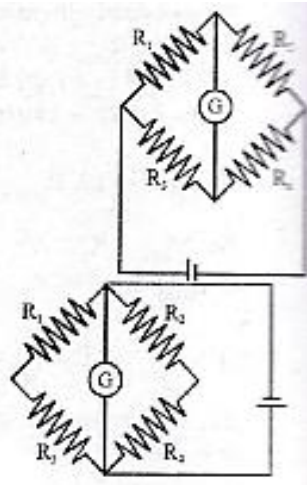

16. (A)

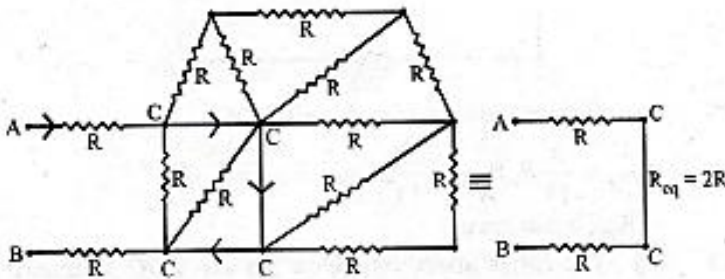(a) Current will follow the path ACCCCB so we will get our final circuit as shown below



17. (B)

(b) Using Kirchhoff's law at P we get


$$\frac{V-12}{1} + \frac{V-13}{2} + \frac{V-0}{10} = 0$$

[Let potential at P, Q, U = 0  
and at R = V]

$$\Rightarrow \frac{V}{1} + \frac{V}{2} + \frac{V}{10} = \frac{12}{1} + \frac{13}{2} + \frac{0}{10}$$

$$\Rightarrow \frac{10+5+1}{10}V = \frac{24+13}{2} \Rightarrow V \left( \frac{16}{10} \right) = \frac{37}{2}$$
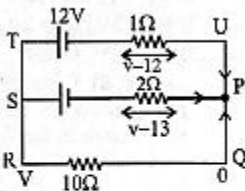
$$\Rightarrow V = \frac{37 \times 10}{16 \times 2} = \frac{370}{32} = 11.56 \text{ volt}$$



18. (A)

(a) Rate of heat i.e., Power developed in the wire

$$P = \frac{V^2}{R}$$

Resistance of the wire of length,  $L$   $R_1 = \frac{\rho L}{A} = \frac{\rho L}{\pi r^2}$

$\therefore$  Power,  $P_1 = \frac{V^2}{R_1}$

Resistance of the wire when length is halved i.e.,  $L/2$

$$R_2 = \frac{\rho \frac{L}{2}}{\pi (2r)^2} = \frac{\rho L}{\pi 8r^2} = \frac{R_1}{8}$$

$\therefore$  Power,  $P_2 = \frac{V^2}{\frac{R_1}{8}} = \frac{8V^2}{R_1}$  or,  $P_2 = 8P_1$

i.e., power increased 8 times of previous or original wire.

19. (B)

Using formula, internet resistance,

$$r = \left( \frac{l_1 - l_2}{l_2} \right) s = \left( \frac{52 - 40}{40} \right) \times 5 = 1.5 \Omega$$

20. (C)

(c)  $R_1 + R_2 = 1000$

$\Rightarrow R_2 = 1000 - R_1$

On balancing condition

$R_1(100 - l) = (1000 - R_1)l$  ... (i)

On Interchanging resistance balance point shifts left by 10 cm.

On balancing condition

$(1000 - R_1)(110 - l) = R_1(l - 10)$

or,  $R_1(l - 10) = (1000 - R_1)(110 - l)$  ... (ii)

Dividing eqn (i) by (ii)

$$\frac{100 - l}{l - 10} = \frac{l}{110 - l}$$

$\Rightarrow (100 - l)(110 - l) = l(l - 10)$

$\Rightarrow 11000 - 100l - 110l + l^2 = l^2 - 10l$



$\Rightarrow 11000 = 200l$  or,  $l = 55$

Putting the value of 'l' in eqn (i)

$R_1(100 - 55) = (1000 - R_1)55 \Rightarrow R_1(45) = (1000 - R_1)55$

$\Rightarrow R_1(9) = (1000 - R_1)11 \Rightarrow 20R_1 = 11000$

$\therefore R_1 = 550 \text{K}\Omega$

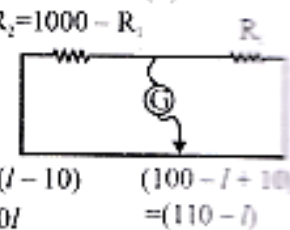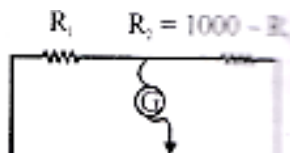



21. (D)

(d) Charge mobility

$$(\mu) = \frac{V_d}{E} \quad [\text{Where } V_d = \text{drift velocity}]$$

$$\text{and resistivity } (\rho) = \frac{E}{j} = \frac{EA}{I} \Rightarrow E = \frac{I(\rho)}{A}$$

$$\Rightarrow \mu = \frac{V_d}{E} = \frac{V_d A}{I \rho} = \frac{1.1 \times 10^{-3} \times \pi \times (5 \times 10^{-3})^2}{5 \times 1.7 \times 10^{-8}}$$

$$\Rightarrow \mu = 1.0 \frac{\text{m}^2}{\text{Vs}}$$

22. (B)

(b) Equation of straight line from graph

$$y = -mx + c$$

$$\Rightarrow \ln R = -m \left( \frac{1}{T^2} \right) + c$$

here, m & c are constants


$$R = e^{-m \left( \frac{1}{T^2} \right) + c} = e^{-m \left( \frac{1}{T^2} \right)} \times e^c \Rightarrow R(T) = R_0 e^{\frac{-T_d^2}{T^2}}$$

23. (A)

$$(a) \quad dR = \frac{(\rho)(dx)}{4\pi x^2}$$

$$R = \int dR$$
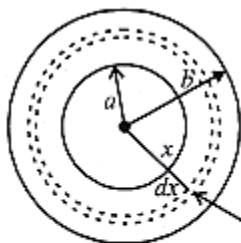
$$\int dR = \rho \int_a^b \frac{dx}{4\pi x^2}$$



$$\Rightarrow R = \frac{\rho}{4\pi} \left[ \frac{-1}{x} \right]_a^b \Rightarrow R = \left( \frac{\rho}{4\pi} \right) \cdot \left( \frac{1}{a} - \frac{1}{b} \right)$$

24. (C)

25. (A)

Clearly, from graph

$$\text{Current, } I = \frac{dq}{dt} = 0 \text{ at } t = 4\text{s} \quad [\text{Since } q \text{ is constant}]$$

26. (A)

Using,  $I = neAv_d$

$$\therefore \text{Drift speed } v_d = \frac{1}{neA}$$


$$= \frac{1.5}{9 \times 10^{28} \times 1.6 \times 10^{-19} \times 5 \times 10^{-6}} = 0.02 \text{ mms}^{-1}$$

27. (C) (c) When length becomes double its resistance becomes

$$(R \propto l^2)$$


$$R = 4 \times 3 = 12 \Omega$$
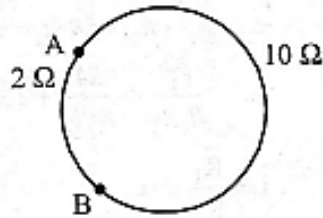
$$R_{\text{eq}} = \frac{2 \times 10}{12} = \frac{5}{3} \Omega$$



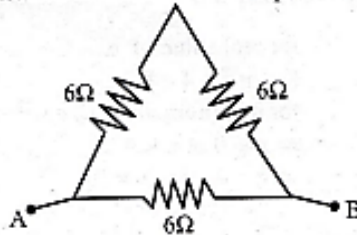28. (A) (a) Resistance,  $R \propto l$  so resistance of each side of the equilateral triangle =  $6 \Omega$

Resistance  $R_{\text{eq}}$  between any two vertices



$$\frac{1}{R_{\text{eq}}} = \frac{1}{12} + \frac{1}{6} \Rightarrow R_{\text{eq}} = 4 \Omega$$

29. (D)


$$(d) \quad i = \left( \frac{\varepsilon}{R+r} \right)$$

Power delivered to R.

$$P = i^2 R = \left( \frac{\varepsilon}{R+r} \right)^2 R$$


$$P \text{ to be maximum, } \frac{dP}{dR} = 0$$
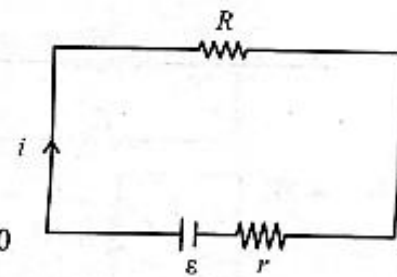
$$\text{or } \frac{d}{dR} \left[ \left( \frac{\varepsilon}{R+r} \right)^2 R \right] = 0 \quad \text{or } R = r$$



30. (B)

(b)

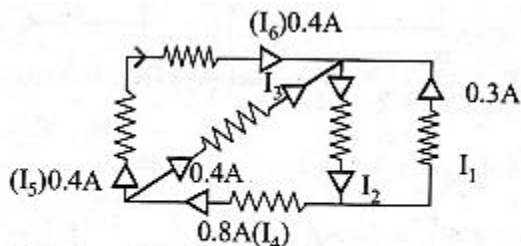

From KCL,  $I_3 = 0.8 - 0.4 = 0.4 \text{ A}$

$$I_2 = 0.4 + 0.4 + 0.3 = 1.1 \text{ A}$$

$$\text{and } I_6 = 0.4 \text{ A}$$

31. (A)

(a) As  $R = \frac{V^2}{P}$ , so  $R_1 = \frac{220^2}{25}$  and  $R_2 = \frac{220^2}{100}$

Current flow  $i = \frac{220}{R_1 + R_2}$

$$P_1 = i^2 R_1 = \frac{220^2}{\left(\frac{220^2}{25} + \frac{220^2}{100}\right)} \times \frac{220^2}{25} = 16 \text{ W}$$

Similarly,  $P_2 = i^2 R_2 = 4 \text{ W}$

32. (B)

(b) When two resistances are connected in series,  
 $R_{eq} = 2R$

Power consumed,  $P = \frac{\epsilon^2}{R_{eq}} = \frac{\epsilon^2}{2R}$

In parallel condition,  $R_{eq} = R/2$ .

New power,  $P' = \frac{\epsilon^2}{(R/2)}$

or  $P' = 4P = 240 \text{ W}$  ( $\because P = 60 \text{ W}$ )

33. (A)

(a) Colour code for carbon resistor

Bl,	Br,	R,	O,	Y,	G,	Blue,	V,	Gr,	W
0	1	2	3	4	5	6	7	8	9

Resistance,  $R = AB \times C \pm D$

$\therefore$  Resistance,  $R = 50 \times 10^2 \Omega$

Now using formula, Power,  $P = i^2 R$

$$\therefore i = \sqrt{\frac{P}{R}} = \sqrt{\frac{2}{50 \times 10^2}} = 20 \text{ mA}$$

34. (A)

(a) Power,  $P = i^2 R$

$4.4 = 4 \times 10^{-6} \times R \Rightarrow R = 1.1 \times 10^6 \Omega$

When supply of 11 v is connected

$$\text{Power, } P' = \frac{v^2}{R} = \frac{11^2}{1.1} \times \frac{11^2}{1.1} \times 10^{-6} = 11 \times 10^{-5} \text{ W}$$

35. (C)

(c) We have given

$$\frac{dR}{d\ell} \propto \frac{1}{\sqrt{\ell}} \Rightarrow \frac{dR}{d\ell} = k \times \frac{1}{\sqrt{\ell}} \quad (\text{where } k \text{ is constant})$$

$$dR = k \frac{d\ell}{\sqrt{\ell}}$$

Let  $R_1$  and  $R_2$  be the resistance of AP and PB respectively.  
Using wheatstone bridge principle

$$\therefore \frac{R'}{R'} = \frac{R_1}{R_2} \text{ or } R_1 = R_2$$

$$\text{Now, } \int dR = k \int \frac{d\ell}{\sqrt{\ell}} \quad \therefore R_1 = k \int_0^{\ell} \ell^{-1/2} d\ell = k \cdot 2 \cdot \sqrt{\ell}$$

$$R_2 = k \int_1^{\ell} \ell^{-1/2} d\ell = k \cdot (2 - 2\sqrt{\ell})$$

Putting  $R_1 = R_2$

$$k2\sqrt{\ell} = k(2 - 2\sqrt{\ell}) \quad \therefore 2\sqrt{\ell} = 1 \Rightarrow \sqrt{\ell} = \frac{1}{2}$$

$$\text{i.e., } \ell = \frac{1}{4} \text{ m} \Rightarrow 0.25 \text{ m}$$

36. (C)

(c) Current flowing through the circuit (I) is given by

$$I = \left( \frac{4}{R+5} \right) \text{ A}$$


$$\text{Resistance of length 10 cm of wire} = 5 \times \frac{10}{100} = 0.5 \Omega$$

According to question,

$$5 \times 10^{-3} = \left( \frac{4}{R+5} \right) \cdot (0.5)$$

$$\therefore \frac{4}{R+5} = 10^{-2} \text{ or } R+5 = 400 \Omega$$

$$\therefore R = 395 \Omega$$

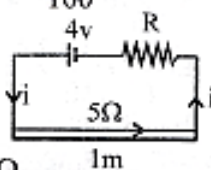

37. (C)

(c) Let  $x$  be the length AJ at which galvanometer shows null deflection current,

$$i = \frac{\epsilon}{12r+r} = \frac{3}{13r} \Rightarrow i \left( \frac{x}{L} 12r \right) = \frac{\epsilon}{2}$$

$$\Rightarrow \frac{\epsilon}{13r} \left[ \frac{x}{L} 12r \right] = \frac{\epsilon}{2} \Rightarrow \frac{\epsilon}{13r} \left[ \frac{x}{L} 12r \right] = \frac{\epsilon}{2} \Rightarrow x = \frac{13L}{24}$$


38. (B)

$$\rho_M = 98 \times 10^{-8}; \rho_A = 2.65 \times 10^{-8}$$

$$\rho_C = 1.724 \times 10^{-8}; \rho_T = 5.65 \times 10^{-8}$$

$$\therefore \rho_M > \rho_T > \rho_A > \rho_C$$

39. (D)

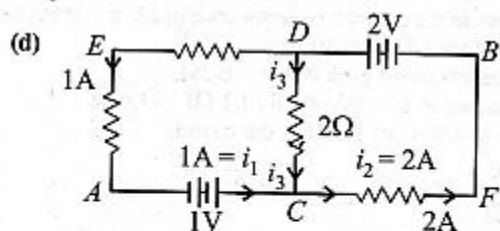

Let us assume the potential at  $A = V_A = 0$   
Using Kirchoff's junction rule at  $C$ , we get

$$i_1 + i_3 = i_2$$

$$1A + i_3 = 2A \Rightarrow i_3 = 2A$$

Now using Kirchoff's loop law along  $ACDB$

$$V_A + 1 + i_3(2) - 2 = V_B$$

$$\Rightarrow V_A + 1 + i_3(1) - 2 = V_B \Rightarrow V_B - V_A = 3 - 2 = 1 \text{ volt}$$

40. (D)

(d) Given : Power,  $P = 1 \text{ kW} = 1000 \text{ W} = P_{\text{output}}$

$$R = 2\Omega, V = 220 \text{ V}$$

$$\text{Current, } I = \frac{P}{V} = \frac{1000}{220}$$

$$P_{\text{loss}} = I^2 R = \left(\frac{1000}{220}\right)^2 \times 2$$

$$P_{\text{in}} = P_{\text{output}} + P_{\text{loss}}$$

$$\therefore \text{Efficiency} = \frac{1000}{1000 + P_{\text{loss}}} \times 100 = 96\%$$


41. (B)

(b) Maximum power in external resistance is generated when it is equal to internal resistance of battery i.e.,  $P_R$  maximum when  $r = R$

The maximum Joule heating in  $R$  will take place for, the resistance of small element

$$dR = \frac{\rho dr}{2\pi r l} \Rightarrow R = \frac{\rho}{2\pi l} \int_a^b \frac{dr}{r}$$
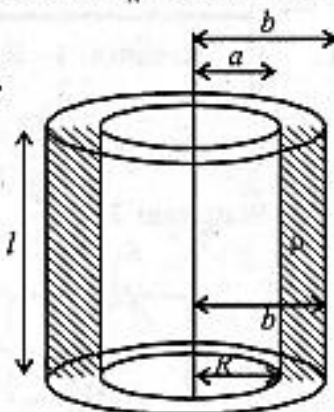
$$\Rightarrow R = \frac{\rho}{2\pi l} \ln \frac{b}{a}$$



42. (D)

(d) The voltmeter of resistance  $10\text{k}\Omega$  is parallel to the resistance of  $400\Omega$ . So, their equivalent resistance is

$$\frac{1}{R'} = \frac{1}{10\text{ k}\Omega} + \frac{1}{400\Omega} = \frac{1}{10000} + \frac{1}{400}$$

$$\Rightarrow \frac{1}{R'} = \frac{1+25}{10000} = \frac{26}{10000} \Rightarrow R' = \frac{10000}{26}\Omega$$

Using Ohm's law, current in the circuit

$$I = \frac{\text{Voltage}}{\text{Net Resistance}} = \frac{6}{\frac{10000}{26} + 800}$$

Potential difference measured by voltmeter

$$V = IR' = \frac{6}{\frac{10000}{26} + 800} \times \frac{10000}{26} \Rightarrow V = \frac{150}{77} = 1.95 \text{ volt}$$

43. (D)

(d) Let  $R$  be the resistance of the whole wire

Potential gradient for the potentiometer wire

$$'AB' = -\frac{dV}{d\ell} = \frac{I \times R}{\ell}$$

$$= \left[ \frac{60 \times R}{\ell_{AB}} \right] \text{mv/m}$$


$$V_{AP} = \left( \frac{dV}{d\ell_{AB}} \right) \ell_{AP}$$

$$= \frac{60 \times R}{1200} \times 1000 \text{mV}$$

$$\Rightarrow V_{AP} = 50 R \text{ mV}$$

Also,  $V_{AP} = 5 \text{ V}$  (for balance point at  $P$ )
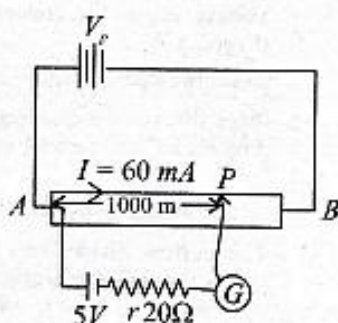
$$\therefore R = \frac{V_{AP}}{50 \times 10^{-3}} = \frac{5}{50 \times 10^{-3}} = 100\Omega$$



44. (D)

(d) From colour code for electric resistance,

Violet Green Red Gold

7 5 2 5%

$$\therefore R = 75 \times 10^2 \pm 5\% \text{ of } 7500 \Rightarrow R = (7500 \pm 375)\Omega$$

45. (A)  
 (a) Current is constant in the conductor.  $I = \text{constant}$

Resistance of element of conductor,  $dR = \frac{\rho dx}{\pi r^2}$


$dV = idR = \frac{i\rho dx}{\pi r^2}$

$E = \frac{dV}{dx} = \frac{i\rho}{\pi r^2}$

Drift velocity,

$V_d = \frac{eE\tau}{m}$  As  $V_d \propto E$  and  $E \propto \frac{1}{r^2}$

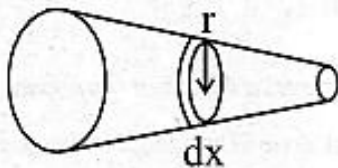So, if  $r$  decreases,  $E$  will increase and hence  $V_d$ .



46. (C)  
 (c) From formula, drift velocity,  $V_d = neV_d\bar{A}$

$\Rightarrow n = \frac{1}{AeV_d} = \frac{10}{5 \times 10^{-6} \times 1.6 \times 10^{-19} \times 2 \times 10^{-3}}$   
 $= 625 \times 10^{25}$

47. (B)  
 (b) Given,  $i = \alpha_0 t + \beta t^2$

Put  $\alpha_0 = 20$  and  $\beta = 8$ , we get  $i = 20t + 8t^2$

Current,  $i = \frac{dq}{dt} \Rightarrow \int dq = \int idt \Rightarrow q = \int_0^{15} (20t + 8t^2) dt$

$\Rightarrow q = \left( \frac{20t^2}{2} + \frac{8t^3}{3} \right)_0^{15} = 20 \times \left( \frac{15^2 - 0^2}{2} \right) + \frac{8}{3} (15^3 - 0^3)$

$\Rightarrow q = 10 \times (15)^2 + \frac{8(15)^3}{3} \Rightarrow q = 2250 + 9000 = 11250 \text{ C}$

48. (B)  
 (b) Resistance,  $R = \frac{\rho \ell}{A} = \frac{\rho \ell^2}{(\text{Vol.})}$  or  $R \propto \ell^2$

or,  $\frac{R_1}{R_2} = \frac{\ell_1^2}{\ell_2^2}$

As length increases 25%, if  $\ell_1 = \ell$  then

$\ell_2 = \ell + \ell \times \frac{25}{100} = 1.25\ell$

$\therefore \frac{R}{R_2} = \frac{\ell^2}{(1.25\ell)^2}$  or,  $R_2 = 1.5625R$

$\therefore$  % increase in resistance  $R = 56\%$

49. (B)

$$(b) R_{net} = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_{net} = \left( \frac{\rho_1 \rho_2}{\rho_1 + \rho_2} \right) \frac{l}{A} \Rightarrow l = \frac{(\rho_i + \rho_A) A R_{net}}{\rho_i \rho_A}$$

Putting the required value we get  $l = 97 \text{ m}$

50. (A)

$$(a) i_r = \frac{25}{5 + R}$$

in parallel,  $E_{eq} = E = 5V$

$$r_{eq} = \frac{r}{5} = \frac{1}{5} \Omega$$

$$i_2 = \frac{5}{R + \frac{1}{5}}$$

putting  $i_1 = i_2$ ,

we get,  $4R = 4 \Rightarrow R = 1 \Omega$ .

51. (A)

(a) Given, Power of electric bulb,  $P = 500W$

$$R = V_1 \Rightarrow 500 = V_1$$

$$\Rightarrow I = 5 \text{ Amp}$$

As current remains same in series, using ohm's law


$$V = I \times R_{eq}$$

$$\Rightarrow 200 = 5 \times R \Rightarrow R_{eq} = 40$$


$$\therefore R + 20 = 40 \Rightarrow R = 20 \Omega$$

52. (B)

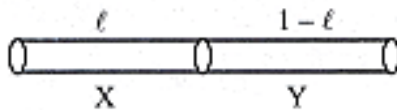(b) Consider of the length of X part is  $\ell$  then the length of Y part will be  $1 - \ell$ .


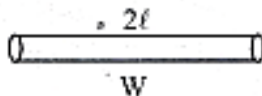
$$\frac{R_X}{R_Y} = \frac{\ell_X}{\ell_Y} \left( \because R = \frac{\rho \ell}{A} \right)$$



When wire is stretched to double of its length, then resistance becomes 4 times.

$$R_W = 4R_X = 2R_Y$$

$$\frac{R_X}{R_Y} = \frac{1}{2} \quad \text{So} \quad \frac{\ell_X}{\ell_Y} = \frac{1}{2}$$



53. (A)

(a) Resistance,  $R_1 = \rho \frac{L_1}{A_1}$

$$R_2 = \rho \left( \frac{3L_1}{A_1/3} \right) = 9\rho \frac{L_1}{A_1} \quad \therefore \frac{R_2}{R_1} = \frac{9\rho \frac{L_1}{A_1}}{\rho \frac{L_1}{A_1}} = 9$$

54. (A)

(a) We know that

$$R = R_0(1 + \alpha\Delta T)$$

So,  $2 = R_0(1 + \alpha \times 10)$  ... (i)

$3 = R_0(1 + \alpha \times 30)$  ... (ii)

Dividing (i) by (ii), we get

$$\frac{3}{2} = \frac{1 + 30\alpha}{1 + 10\alpha} \Rightarrow 3 + 30\alpha = 2 + 60\alpha \Rightarrow 1 = 30\alpha$$

$$\Rightarrow \alpha = \frac{1}{30} = 0.033 \text{ } ^\circ\text{C}^{-1}$$

55. (C)

$$R = \frac{\rho l}{A}$$

$$\frac{\Delta R}{R} = \frac{\Delta l}{l} - \frac{\Delta A}{A}$$

[Note: This is not relative error case, so -ve sign comes

with  $\frac{\Delta A}{A}$ ]

Now,  $V = \text{constant}$

$$Al = \text{constant}$$

$$\Rightarrow \frac{\Delta A}{A} + \frac{\Delta l}{l} = 0 \Rightarrow -\frac{\Delta A}{A} = \frac{\Delta l}{l}$$

$$\text{So, } \frac{\Delta R}{R} = \frac{\Delta l}{l} + \frac{\Delta l}{l} \left[ \because \frac{\Delta l}{l} = -\frac{\Delta A}{A} \right]$$

$$= \frac{2\Delta l}{l} = 2 \times 0.4 = 0.8\%$$

56. (B)

(b)  $A \left( \begin{array}{c} \sigma_1 \\ l \end{array} \right) \left( \begin{array}{c} \sigma_2 \\ l \end{array} \right) \equiv \left( \begin{array}{c} \sigma_{eq} \\ 2l \end{array} \right) A$

Let length of wire be ' $l$ ' and area of wire as ' $A$ '

For equivalent wire length =  $2l$ ; area will be  $A$

Equivalent thermal resistance in series will be given as

$$R_{eq} = R_1 + R_2$$

$$\Rightarrow \frac{2\ell}{\sigma_{eq} A} = \frac{\ell}{\sigma_1 A} + \frac{\ell}{\sigma_2 A} \quad \left[ \because R = \frac{\ell}{\sigma A} \right]$$

$$\Rightarrow \frac{2\ell}{\sigma_{eq}} = \frac{\ell}{\sigma_1} + \frac{\ell}{\sigma_2} \Rightarrow \sigma_{eq} = \frac{2\sigma_1\sigma_2}{\sigma_1 + \sigma_2}$$


57. (B)

(b) As  $R = \frac{\rho l}{A} \Rightarrow R_i = 14\Omega = \frac{\rho l_0}{\pi r_0^2}$

$$R_f = \frac{\rho l_0}{\pi \left(\frac{r_0}{3}\right)^2} = 9 \frac{\rho l_0}{\pi r_0^2} = 9R_i = 9 \times 14 = 126\Omega$$

$$R_{eq} = \frac{R_f}{7} = \frac{126}{7} = 18\Omega$$

58. (A)

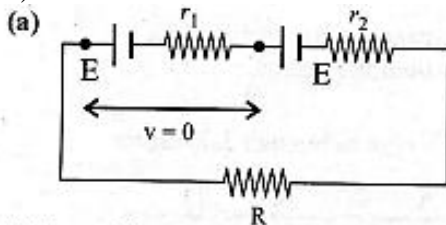

We have,  $E - ir_1 = 0$   $[\because V_{r_1} = 0]$   
 $\Rightarrow E - ir_1 = 0$

Now,  $i = \frac{2E}{r_1 + r_2 + R}$

$$\Rightarrow \frac{E}{r_1} = \frac{2E}{r_1 + r_2 + R} \quad \left[ \because i = \frac{E}{r_1} \right]$$

$$\Rightarrow r_1 + r_2 + R = 2r_1$$

$$\Rightarrow R = r_1 - r_2$$

59. (A)

(a) In series

$$i_s = \frac{2E}{2r + 2}$$



In parallel

$$i_p = \frac{E}{\frac{r}{2} + 2} = \frac{2E}{r + 4}$$

as,  $i_s = i_p$

$$\Rightarrow \frac{2E}{2r + 2} = \frac{2E}{r + 4}$$

$$\Rightarrow r = 2\Omega$$

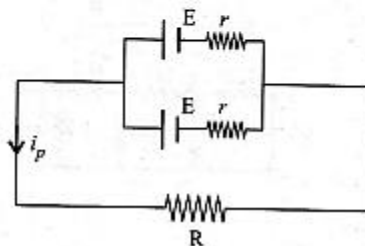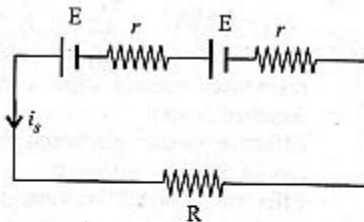

60. (A)

We, have,

$$i = \frac{E_{net}}{R_{net}} = \frac{2E}{R + x_1 + x_3}$$


As. P.d across second cell = 0

$$\Rightarrow E - ir_2 = 0 \quad [\because V = E - iR]$$

$$\Rightarrow E - \frac{2Er_2}{R + r_1 + r_2} = 0$$

$$\Rightarrow R + r_1 + r_2 - 2r_2 = 0$$

$$\Rightarrow R = r_2 - r_1$$

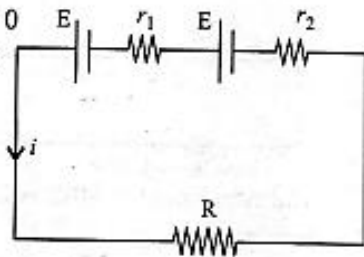

61. (C)



(c) Statement 1 -  $R = 80 \Omega$

$$R_1 = R_2 = R_3 = R_4 = 20 \Omega$$

$$\text{In parallel } R_{eq} = \frac{20}{4} = 5 \Omega$$

Statement 2 -

$$R_1 = 3R$$

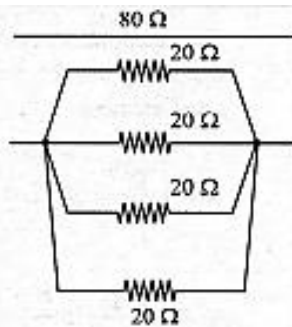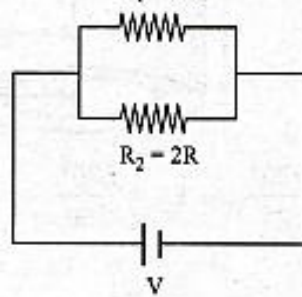

$$P_{th} = \frac{V^2}{R} \Rightarrow P \propto \frac{1}{R}$$

$$\text{So, } \frac{P_1}{P_2} = \left( \frac{R_2}{R_1} \right) = \frac{2}{3} \quad (\text{where } P \text{ is power})$$

62. (B)

(b) Given


$$\frac{1}{2} \frac{\Delta U}{\Delta t} = P_{Bulb} \times N, \text{ where } N = \text{no. of bulb}$$

$$\Rightarrow \frac{9 \times 10^4 \times 10 \times 40}{2 \times 3600} = 100 \times N \quad \left[ \because \frac{\Delta U}{\Delta t} = \frac{mgh \text{ J}}{3600 \text{ S}} \right]$$

$$\Rightarrow N = \frac{36 \times 10^6}{72 \times 10^4} \Rightarrow N = \frac{1}{2} \times 100 \Rightarrow N = 50$$

63. (A)

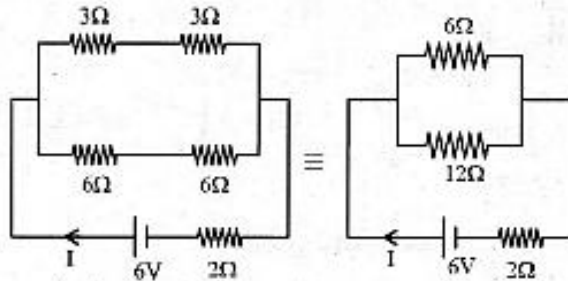(a) Balanced wheat stone bridge in circuit so there is no current in  $5\Omega$  resistor so it can be removed from the circuit.



The equivalent resistance will be

$$R_{eq} = \frac{6 \times 12}{6 + 12} + 2 = 6 \Omega$$

Now, apply K.V.L, we have

$$I = \frac{V}{R_{eq}} = \frac{6}{6} = 1A$$

64. (2)

(2) Current through  $AB$ ,  $i_1 = \frac{40}{40 + 60} = 0.4$


Current through  $AD$ ,  $i_2 = \frac{40}{90 + 110} = \frac{1}{5}$

Using KVL in BAD loop

$$V_B + i_1(40) - i_2(90) = V_D$$


$$\Rightarrow V_B - V_D = \frac{1}{5}(90) - \frac{4}{10}(40)$$

$$\Rightarrow V_B - V_D = 18 - 16 = 2V$$

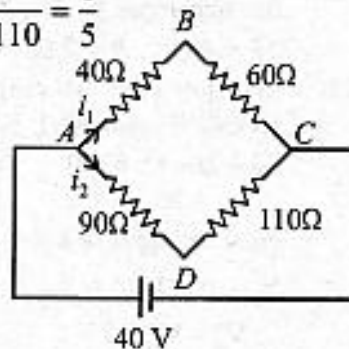

65. (30.00)

(30.00)

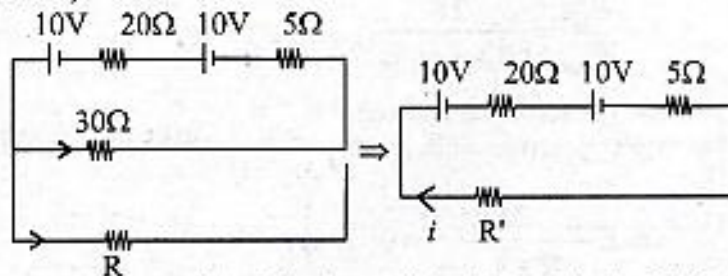

The resistance of  $30\Omega$  is in parallel with  $R$ . Their effective resistance

$$\frac{1}{R'} = \frac{1}{30} + \frac{1}{R} \Rightarrow R' = \frac{30R}{30+R}$$

Now,  $10 - i \times 20 = 0$   
 $i = 0.5 \text{ A}$

as,  $i = \frac{E}{R_{\text{eq}}} \Rightarrow 0.5 = \frac{10+10}{R'+25}$

$$\Rightarrow 0.5 = \frac{20}{\frac{30R}{R+30} + 25} \Rightarrow R = 30\Omega$$

66. (12)

(12) We know that

$E \propto \ell$  where  $\ell$  is the balancing length

$$\therefore E = k(560) \quad \dots(i)$$

When the balancing length changes by 60 cm

$$\frac{E}{r+10} = k(500) \quad \dots(ii)$$

Dividing (i) by (ii) we get


$$\Rightarrow \frac{r+10}{10} = \frac{56}{50} \Rightarrow 50r + 500 = 560$$

$$\Rightarrow r = \frac{6}{5}\Omega = \frac{N}{10}\Omega \Rightarrow N = 12$$

67. (1)

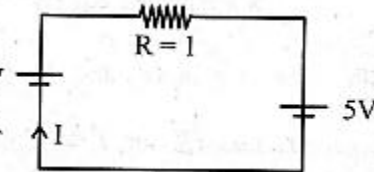(1) From graph (figure 1)  
 voltage at  $t = 3.2\text{s} = 6\text{V}$

$$\text{Current, } I = \frac{V}{R} = \frac{6-5}{1} = 1\text{A}$$



68. (4)

(4)  $I_1 = I_2 = I_{\text{eq}}$   
 $A_1 = A_2 = A$  and  $A_{\text{eq}} = 2A$

$$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2} \Rightarrow \frac{\rho(l)}{2A} = \frac{\left(\frac{\rho_1 l}{A}\right)\left(\frac{\rho_2 l}{A}\right)}{\frac{\rho_1 l}{A} + \frac{\rho_2 l}{A}}$$

$$\Rightarrow \frac{\rho}{2} = \frac{\rho_1 \rho_2}{\rho_1 + \rho_2} \Rightarrow \frac{\rho}{2} = \frac{\rho_1 \rho_2}{(\rho_1 + \rho_2)} = \frac{6 \times 3}{(6+3)} = 2$$

$$\therefore \rho = 4$$

69. (5)

(5) Given : Conductivity of wire,  $\sigma = 5 \times 10^7 \text{ S/m}$

Radius of wire,  $r = 0.5 \text{ mm} = 5 \times 10^{-4} \text{ m}$

Electric field,  $E = 10 \times 10^{-3} \text{ V/m}$

$$J = \sigma E = 10 \times 10^{-3} \times 5 \times 10^7 \Rightarrow J = 5 \times 10^5$$

$$\text{Since, } J = \frac{i}{A} \Rightarrow \frac{i}{A} = 5 \times 10^5$$

$$\Rightarrow i = 5 \times 10^5 \times \pi r^2 = 5 \times 10^5 \times \pi \times (5 \times 10^{-4})^2 \\ = 125\pi \times 10^{-3} \text{ A}$$

$$\therefore i = 125\pi \text{ mA} \quad \therefore i = 5^3 \pi \text{ mA} \quad \therefore x = 5$$

70. (300)

(300) Given,

Charge,  $q = 20 \text{ C}$ , potential difference,  $\Delta V = 15 \text{ V}$

Work done,  $W = q\Delta V = 20 \times 15 = 300 \text{ J}$

71. (4)

(4) Equivalent resistance in series,  $s = R_1 + R_2$

Equivalent resistance in parallel  $P = \frac{R_1 R_2}{R_1 + R_2}$

$$\text{Given } (R_1 + R_2) = n \left( \frac{R_1 R_2}{R_1 + R_2} \right)$$

$$\Rightarrow R_1^2 + R_2^2 + 2R_1 R_2 = n R_1 R_2$$

$$\Rightarrow \frac{R_1^2}{R_1 R_2} + \frac{R_2^2}{R_1 R_2} + 2 = n \Rightarrow \frac{R_1}{R_2} + \frac{R_2}{R_1} + 2 = n$$

$$\text{Let } \frac{R_1}{R_2} = \alpha$$

$$\text{Then, } \alpha + \frac{1}{\alpha} + 2 = n \Rightarrow \alpha^2 + \alpha(2 - n) + 1 = 0$$

for real value of ' $\alpha$ '

$$(2 - n)^2 - 4 \geq 0$$

$$\text{for minimum value } (2 - n)^2 - 4 = 0$$

$$\Rightarrow n = 0 \text{ or } n = 4$$

$$\Rightarrow n = 4 \quad [\because n \neq 0]$$

72. (20)

(20) in series current  $i_1$  will be  $i_1 = \frac{20}{10+10n} = \frac{2}{1+n}$

Current in parallel will be  $i_2 = \frac{20}{\frac{10}{n}+10} = \frac{2}{1+n}$

$$\frac{i_2}{i_1} = 20 \Rightarrow \frac{\left(\frac{2n}{1+n}\right)}{\left(\frac{2}{1+n}\right)} = 20 \Rightarrow n = 20$$

73. (15)

(15) Here,  $I = \frac{E}{R+r}$   $\therefore$  Terminal voltage  $v = IR = \frac{ER}{R+r}$

When potential difference,  $V = 1.25\text{V}$  and  $R_L = 5\Omega$ , then

$$1.25 = \frac{E(5)}{5+r} \quad \dots(i)$$

when potential difference  $V = 1\text{V}$  and  $R_L = 2\Omega$  then

$$I = \frac{E(2)}{2+r} \quad \dots(ii)$$

From eq. (i) and (ii)

we get  $E = \frac{3}{2} = \frac{15}{10}$   $\therefore$  value of  $x = 15$

74. (4)

(4) First case  $P_1 = \frac{V^2}{R} = \frac{(240)^2}{36}$

Second case  $P_2 = \frac{V^2}{R/2} \times 2 = \frac{4v^2}{R} = \frac{4 \times (240)^2}{36}$

$$\therefore \frac{P_1}{P_2} = \frac{1}{4} \quad x = 4.00$$

75. (3840)

(3840) Rate of energy dissipated

$$= \frac{192J}{15} = i^2 R \Rightarrow 192 = 42 \times R, R = 12\Omega$$

$$\text{Energy} = i^2 R t = (8)^2 \times 12 \times 5 = 3840 J$$

76. (2500)

(2500) From,  $H = i^2 R \Delta T$

$$10 \times 10^{-3} = (2 \times 10^{-3})^2 \times R \times 1 \quad \therefore R = 2500 \Omega$$

77. (48)


(48) In balanced condition,

$$\frac{x}{12} = \frac{72-x}{6}$$

$$\Rightarrow x = 2(72 - x)$$

$$\text{or, } 3x = 144$$
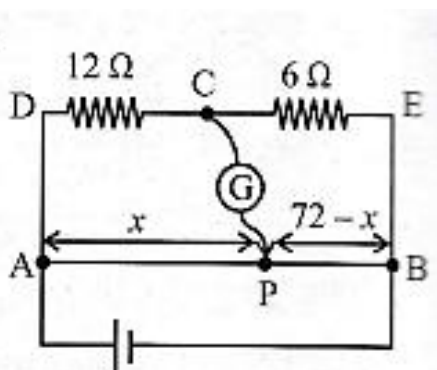
$$\therefore x = \frac{144}{3} = 48 \text{ cm}$$



78. (144)

(144) We have

$$R = \text{slope of } I-V \text{ curve} = \tan 45^\circ = 1$$

$$\text{As, } R = \frac{\rho l}{A} \Rightarrow \rho = \frac{RA}{l} = \frac{1 \times \pi \times (1.2 \times 10^{-2})^2}{31.4 \times 10^{-2}}$$

$$= 144 \times 10^{-3} \Omega \text{ cm}$$

79. (48)

(48)  $I = J A$

$$= 4 \times 10^6 \left[ \pi R^2 - \pi \left( \frac{R}{2} \right)^2 \right] = 4\pi \times 10^6 \left[ \frac{3R^2}{4} \right]$$

$$= \pi \times 10^6 \times 3 \times 16 \times 10^{-6} = 48 \pi \text{ A}$$

80. (300)

(300) If length is increased by  $n$  times then, resistance increased by  $n^2$  times

$$\text{So, } R_f = 4R_i$$


$$\Delta R = R_f - R_i = 3R_i$$

$$\% \Delta R = \frac{3R_i}{R_i} \times 100 = 300\%$$



81. (2)

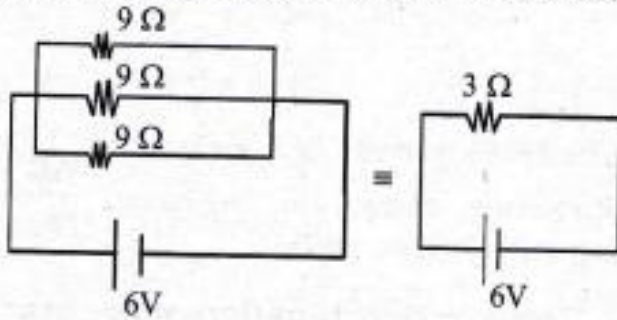(2) Equivalent circuit of the above circuit is as shown below



$$I = \frac{6}{3} = 2\text{A}$$


82. (10)

We have  $i = \frac{15}{1+2} = 5\text{A}$

And,  $V_A = V_B = -15 + iR = -15 + 5 \times 1 = -10\text{V}$

So,  $V_B - V_A = 10\text{V}$ .

83. (8)

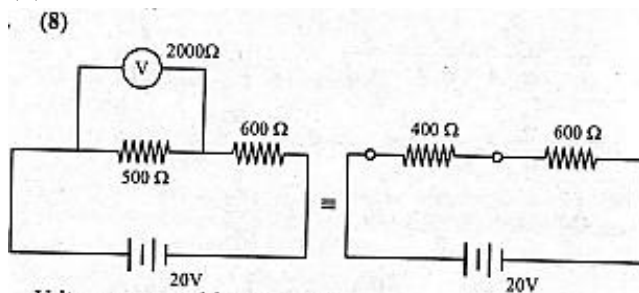

Voltage measured by voltmeter  
= voltage across  $400\ \Omega$

$$= \frac{400}{400 + 600} \times 20 = 8\text{V}$$

84. (4)

$$(4) \quad E_{\text{eq}} = \frac{\frac{E_1}{r_1} + \frac{E_2}{r_2} + \frac{E_3}{r_3}}{\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3}} = \frac{\frac{2}{1} + \frac{4}{1} + \frac{4}{1}}{\frac{1}{1} + \frac{1}{1} + \frac{1}{1}} = \frac{12}{3}\text{V}$$

$$r_{\text{eq}} = \frac{1}{3}\text{k}\Omega$$

So,  $V_o = E_{\text{eq}} - i r_{\text{eq}} = \frac{12}{3} - 0 \times \frac{1}{3} = 4\text{V}$

85. (14)

For Bulb 1

$$R_1 = \frac{V^2}{P} = \frac{220^2}{100} = 484$$

For Bulb 2

$$R_2 = \frac{V^2}{P} = \frac{220^2}{60} = 484 \left( \frac{10}{6} \right)$$

$$I = \frac{220}{484 + 484 \times \frac{10}{6}} \quad \left[ \because I = \frac{E}{R_1 + R_2} \right]$$
$$P_1 = I^2 R_1 = 14.06 \text{ W}$$

86. (15)

(15) Thermal energy,  $H = \frac{V^2}{R} t$

$$\text{So, } H = \frac{V^2}{R_1} \times 20 \quad \dots(i)$$

$$H = \frac{V^2}{R_2} \times 60 \quad \dots(ii)$$

Dividing (ii) by (i), we get

$$1 = \frac{R_2}{R_1} \times \frac{1}{3} \Rightarrow R_2 = 3R_1$$

$$\text{Now, as } H = \frac{V^2}{R_{eq}} \times t \Rightarrow \frac{V^2}{R_1} \times 20 = \frac{V^2 \times t}{R_{eq}} \quad [\text{from (i)}]$$

$$\Rightarrow \frac{20}{R_1} = \frac{t}{3R_1} \quad \left[ \because R_{eq} = \frac{R_1 \cdot 3R_1}{R_1 + 3R_1} \right]$$

$$\Rightarrow t = 15 \text{ minutes}$$

87. (975)

(975) As,  $P = Vi$

$$\Rightarrow 5 = 25i \Rightarrow i = 0.2A$$

$$\text{Now, } i = \frac{V_R}{R} \Rightarrow 0.2 = \frac{220 - 25}{R}$$

$$R = \frac{195}{0.2} = 975 \Omega$$


88. (780)

(780) Given null point for cell is,  $AC = 60$  cm and  $AB = 300$  cm

$$E = \frac{AC}{AB}(V_A - V_B)$$

$$\therefore 20 \times 10^{-3} = \frac{60}{300} \times \frac{4 \times 20}{R + 20}$$


$$\therefore R = 780 \Omega$$

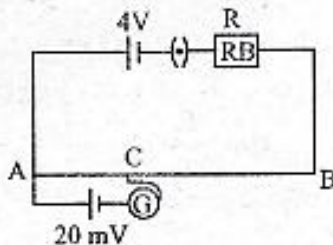

89. (20)

(20) Let resistance of potentiometer wire is  $R$ . The current in the circuit,

$$i = \frac{4}{R + 780}$$

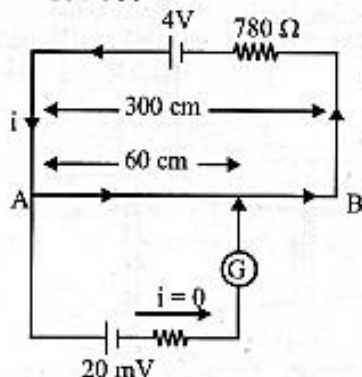

Potential difference across  $AB$ ,  $V_{AB} = iR$

$$= \frac{4}{R + 780}$$

Potential difference across  $AC$ ,  $V_{AC} = iR$

$$= \frac{4R \times 60}{(R + 780) \times 300} = \frac{4R}{5(R + 780)}$$

This should be equal to 20 mV.

$$\frac{4R}{5(R + 780)} = 20 \times 10^{-3} \Rightarrow 4R = 5 \times 20 \times 10^{-3} (R + 780)$$

$$\Rightarrow 40R = R + 780 \Rightarrow 39R = 780$$

$$R = \frac{780}{39} = 20 \Omega$$

90. (54)

(54) As,  $E = K\ell$

$$1.2 = (\text{Potential Gradient}) \times 36$$

$$1.8 = (\text{Potential Gradient}) \times x$$


On dividing, we get

$$\frac{2}{3} = \frac{36}{x} \Rightarrow x = 18 \times 3 = 54 \text{ cm}$$

91. (8)

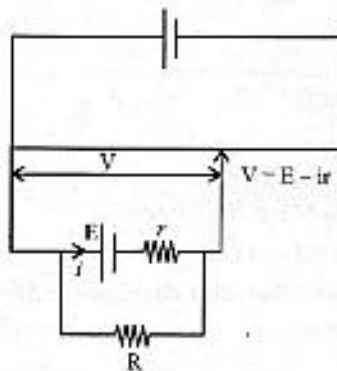(8) We have

$$\frac{V_1}{V_2} = \frac{K \times 3}{K \times 2} = \frac{3}{2}$$



$$\text{Also, } \frac{V_1}{V_2} = \frac{E - i_1 r_1}{E - i_2 r_2} = \frac{E - \frac{E}{8+r} \times r}{E - \frac{E}{4+r} \times r}$$

$$\frac{V_1}{V_2} = \frac{8(4+r)}{4(8+r)}$$


From (i) & (ii), we get

$$\frac{3}{2} = \frac{8(4+r)}{4(8+r)} \Rightarrow \frac{3}{4} = \frac{4+r}{8+r}$$

$$\Rightarrow 24 + 3r = 16 + 4r \Rightarrow 8 = r \Rightarrow r = 8\Omega$$

92. (25)

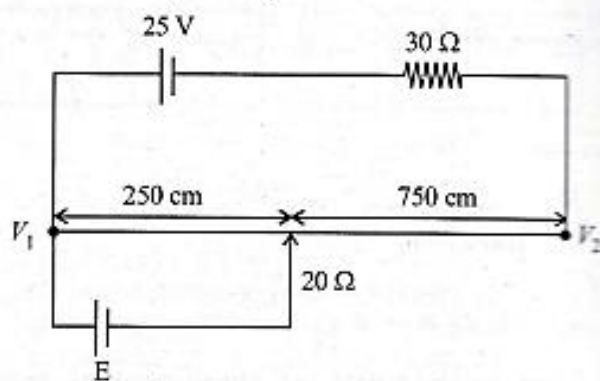(25) Current  $i = \frac{25V}{(30 + 20)\Omega}$



$$\Rightarrow i = 0.5A$$

$$\text{So, } v_1 - v_2 = 20i = 20 \times 0.5 = 10 \text{ v}$$

$$E = \text{Potential gradient} \times 250 = \frac{10}{1000} \times 250$$

$$= 2.5 \text{ V} = \frac{25}{10} \text{ V}$$